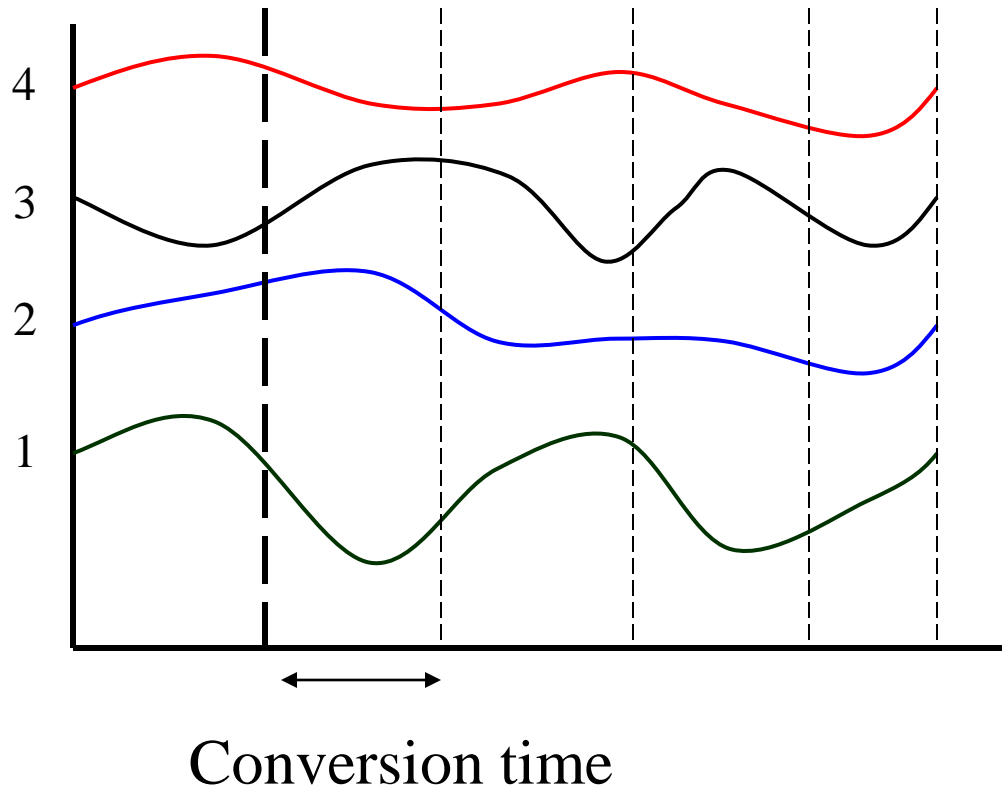



AE 242
Aerospace Measurements
Laboratory

Timing for various ADCs




ADC

One Multiplexer, sample and hold, ADC


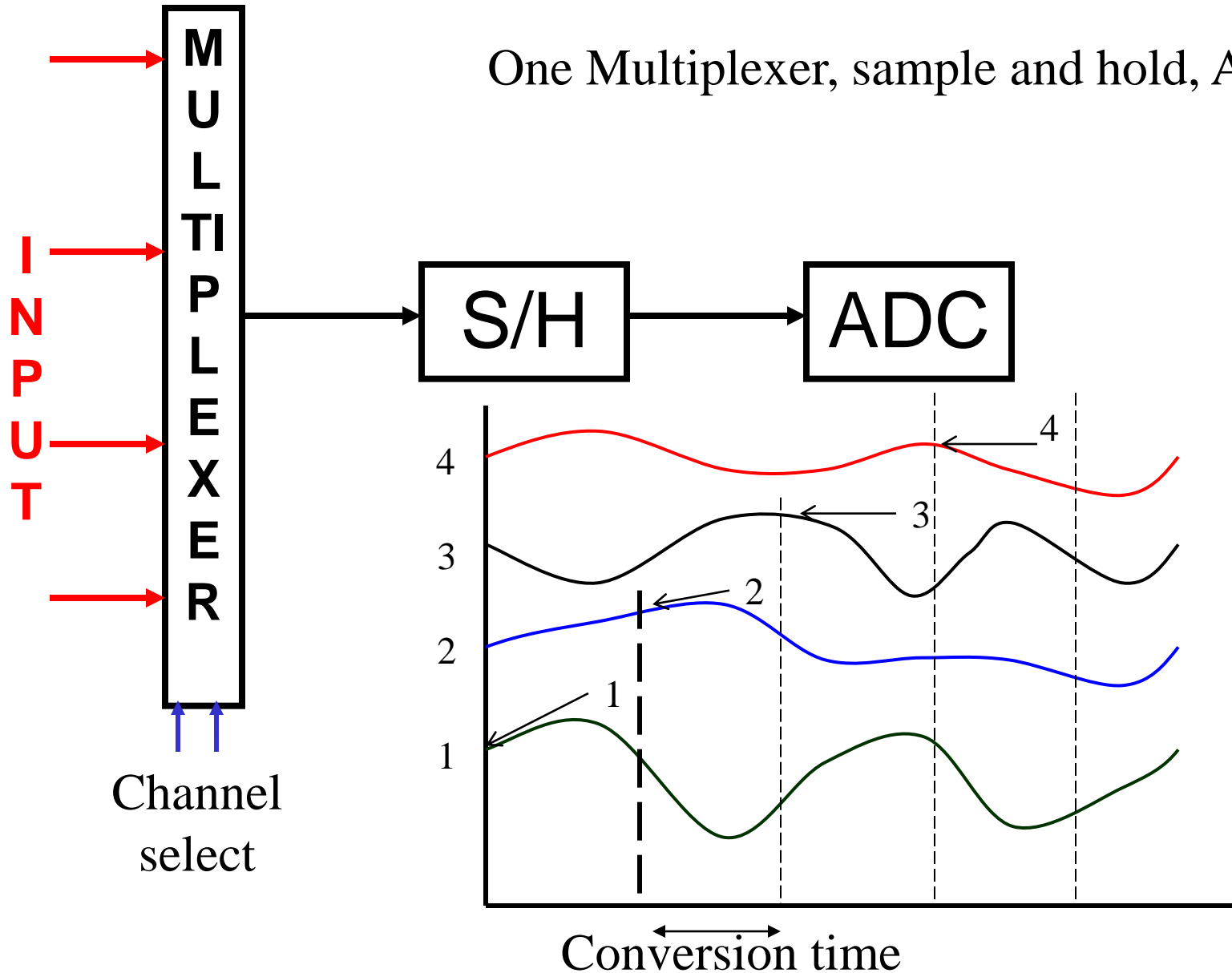


ADC

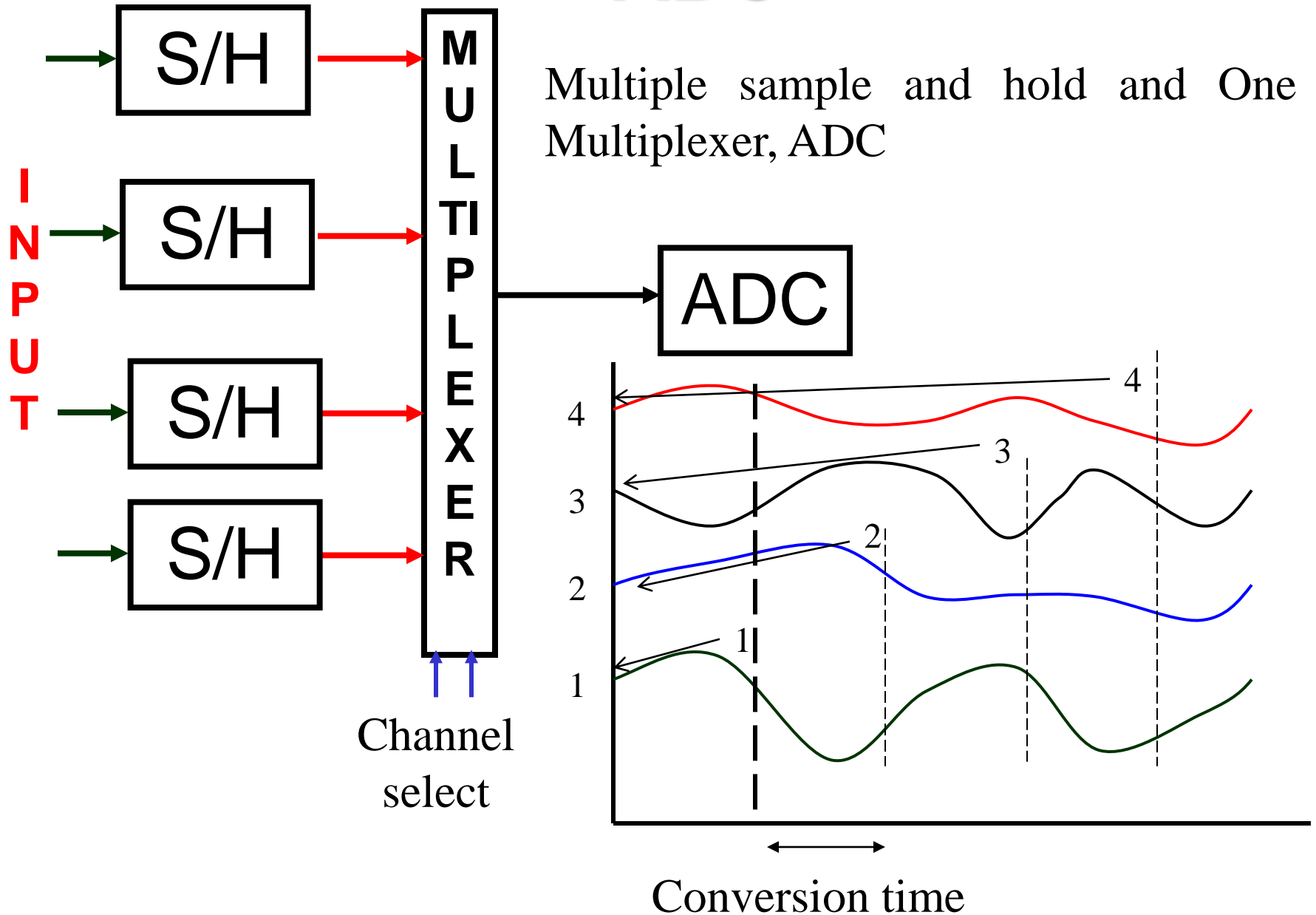


ADC

Multiple sample and hold and ADCs

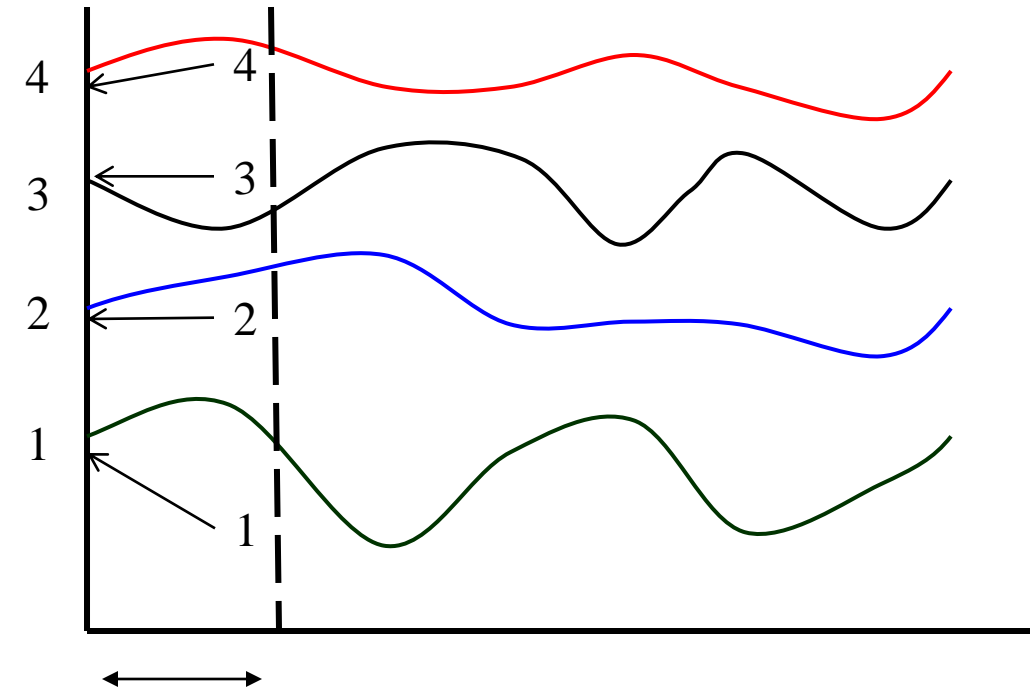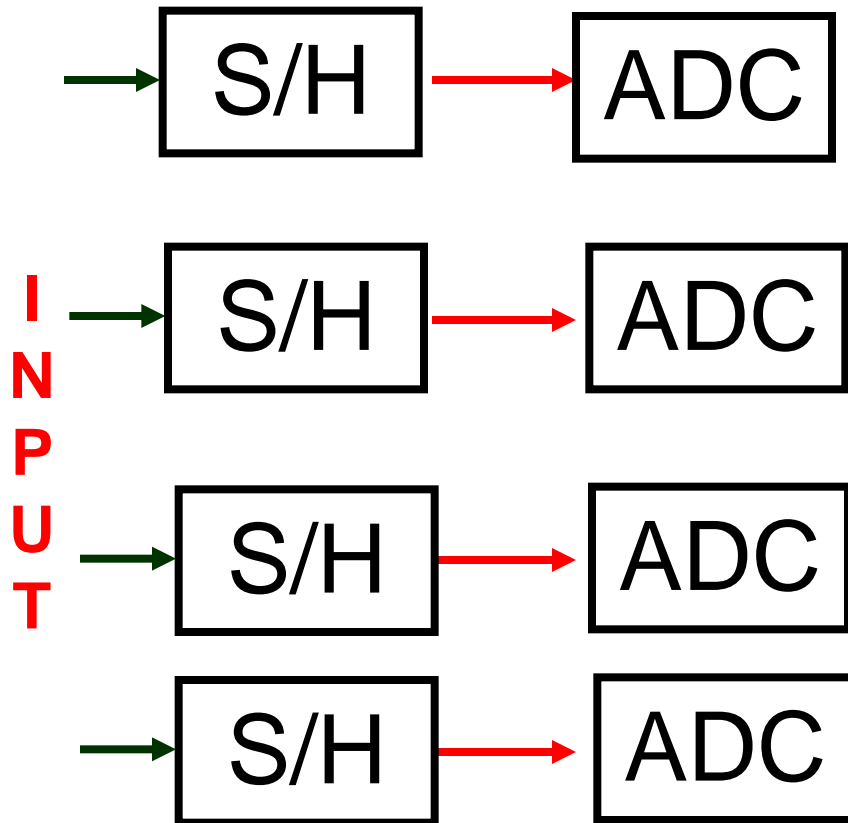


Conversion time

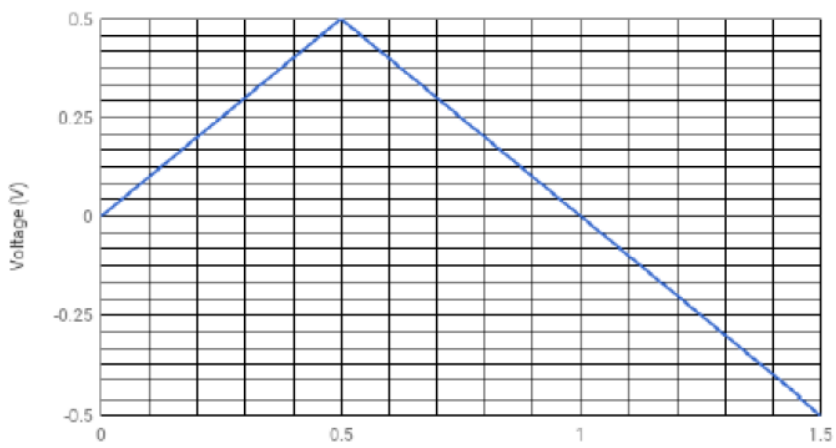Q1) Figure given below shows a voltage changing with time. This voltage is given as input to a two channel analog to digital conversion system (at any given instant both input channel will same voltage. System a) one two channel multiplexer +One sample and hold + one ADC connected in series. System b) Two sample and hold + one two channel multiplexer + One ADC. Assume ADC conversion time as 0.1 sec , 0 digital value is for 0 volt and 500 digital value is equal to 0.5 V. Fill the values of ADC recorded at the given time instants. (6)





Time	Voltage	case-a		case-b	
		Channel1	Channel2	Channel1	Channel2
0	0				
0.1	0.1				
0.2	0.2				
0.3	0.3				
0.4	0.4				
0.5	0.5				
0.6	0.4				
0.7	0.3				
0.8	0.2				
0.9	0.1				
1	0				
1.1	-0.1				
1.2	-0.2				
1.3	-0.3				
1.4	-0.4				
1.5	-0.5				

ADC

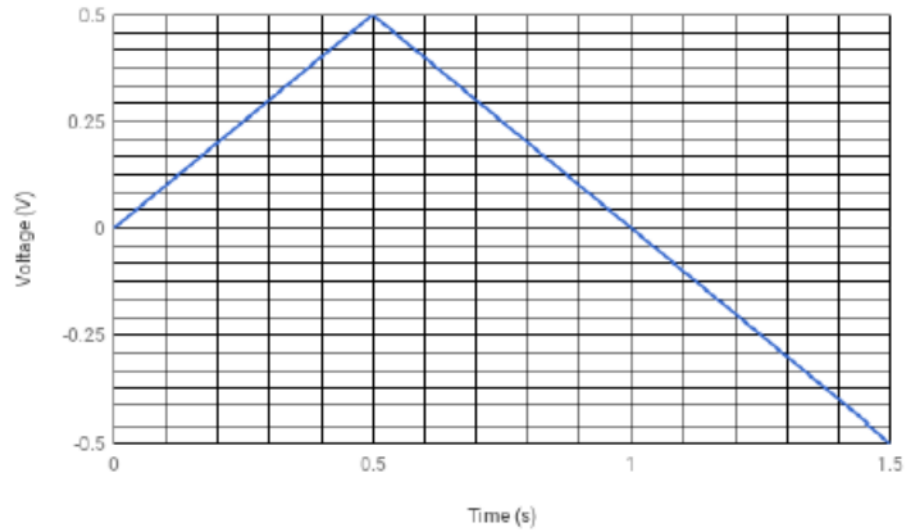


Time	Voltage	case-a		case-b	
		Channel1	Channel2	Channel1	Channel2
0	0				
0.1	0.1				
0.2	0.2				
0.3	0.3				
0.4	0.4				
0.5	0.5				
0.6	0.4				
0.7	0.3				
0.8	0.2				
0.9	0.1				
1	0				
1.1	-0.1				
1.2	-0.2				
1.3	-0.3				
1.4	-0.4				
1.5	-0.5				

ADC

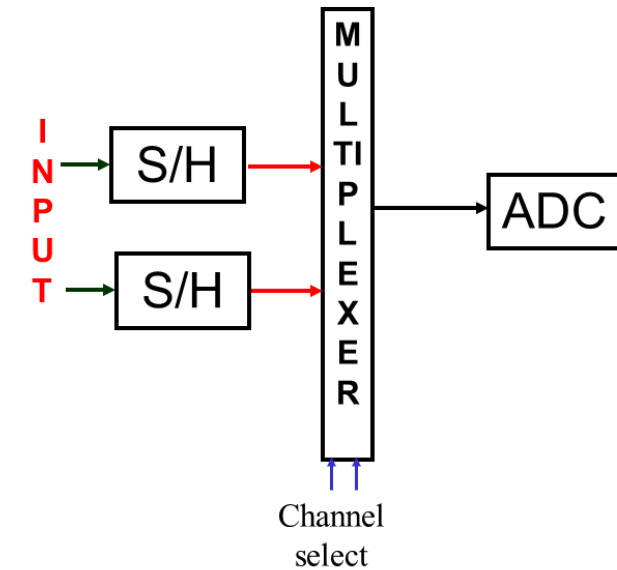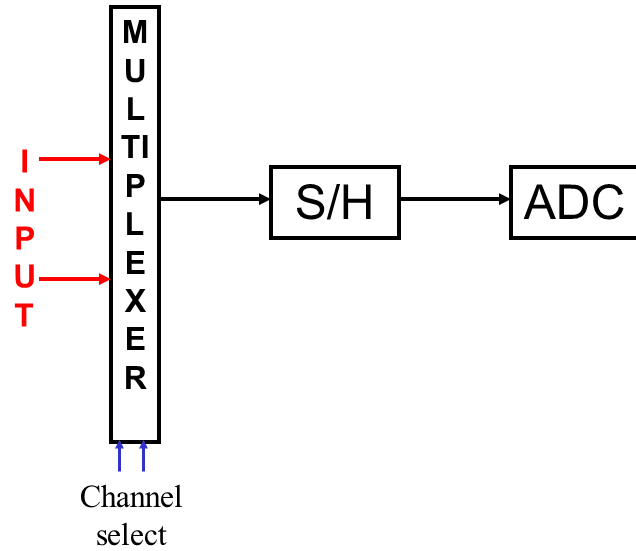


Time	Voltage	case-a		case-b	
		Channel1	Channel2	Channel1	Channel2
0	0				
0.1	0.1				
0.2	0.2				
0.3	0.3				
0.4	0.4				
0.5	0.5				
0.6	0.4				
0.7	0.3				
0.8	0.2				
0.9	0.1				
1	0				
1.1	-0.1				
1.2	-0.2				
1.3	-0.3				
1.4	-0.4				
1.5	-0.5				

ADC

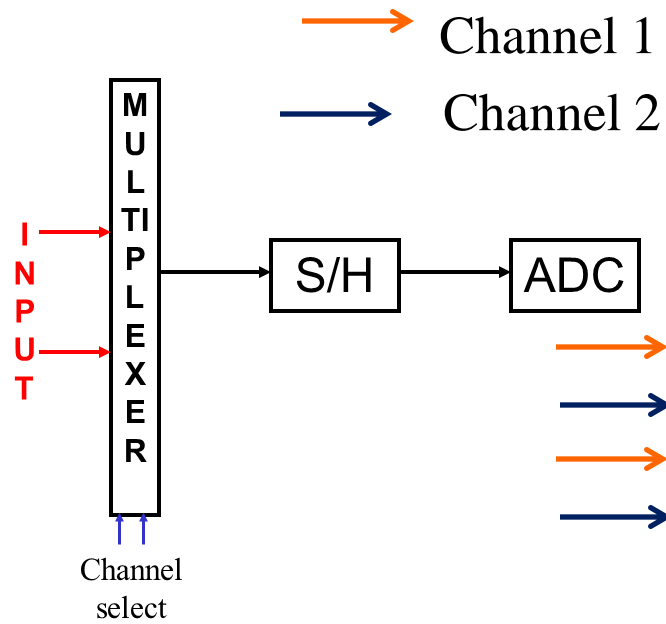


Time	Voltage	case-a		case-b	
		Channel1	Channel2	Channel1	Channel2
0	0	0	0	0	0
0.1	0.1	0	0		
0.2	0.2	0	0.1		
0.3	0.3	0.2	0.1		
0.4	0.4	0.2	0.3		
0.5	0.5		0.3		
0.6	0.4				
0.7	0.3				
0.8	0.2				
0.9	0.1				
1	0				
1.1	-0.1				
1.2	-0.2				
1.3	-0.3				
1.4	-0.4				
1.5	-0.5				


ADC

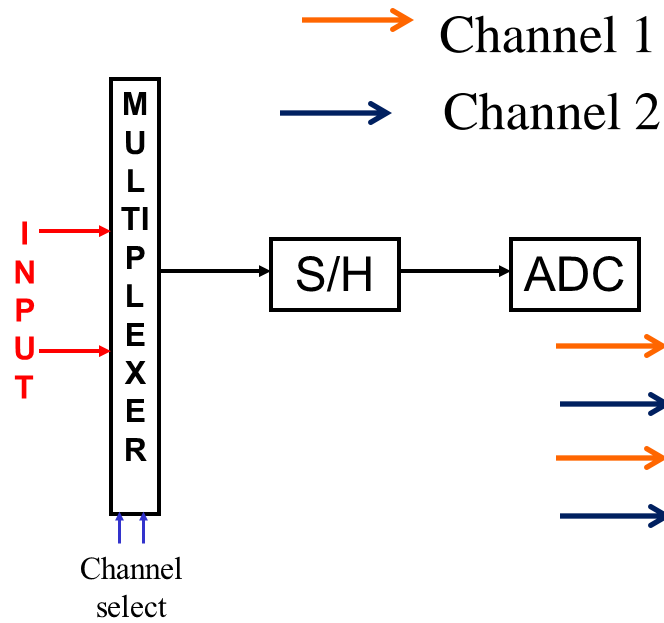

Time	Voltage	case-a		case-b	
		Channel1	Channel2	Channel1	Channel2
0	0	0	0	0	0
0.1	0.1	0	0		
0.2	0.2	0	0.1		
0.3	0.3	0.2	0.1		
0.4	0.4	0.2	0.3		
0.5	0.5		0.3		
0.6	0.4				
0.7	0.3				
0.8	0.2				
0.9	0.1				
1	0				
1.1	-0.1				
1.2	-0.2				
1.3	-0.3				
1.4	-0.4				
1.5	-0.5				

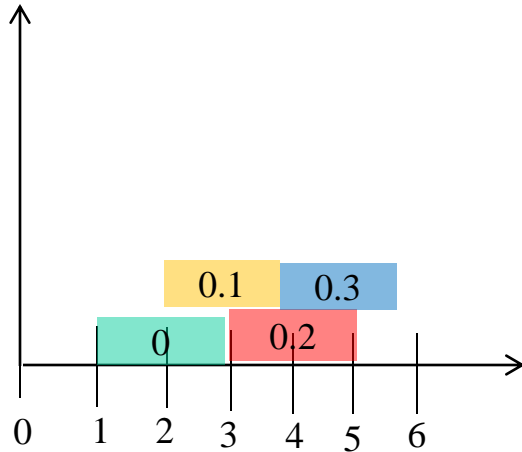

→ S/H Channel 1 and Channel 2

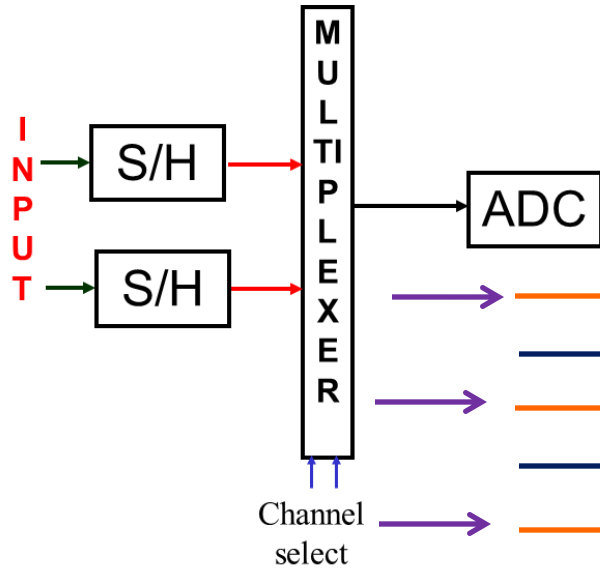

Time	Voltage	case-a		case-b	
		Channel1	Channel2	Channel1	Channel2
0	0	0	0	0	0
0.1	0.1	0	0		
0.2	0.2	0	0		
0.3	0.3	0.2	0		
0.4	0.4	0.2	0.2		
0.5	0.5	0.4	0.2		
0.6	0.4	0.4	0.4		
0.7	0.3		0.4		
0.8	0.2				
0.9	0.1				
1	0				
1.1	-0.1				
1.2	-0.2				
1.3	-0.3				
1.4	-0.4				
1.5	-0.5				

