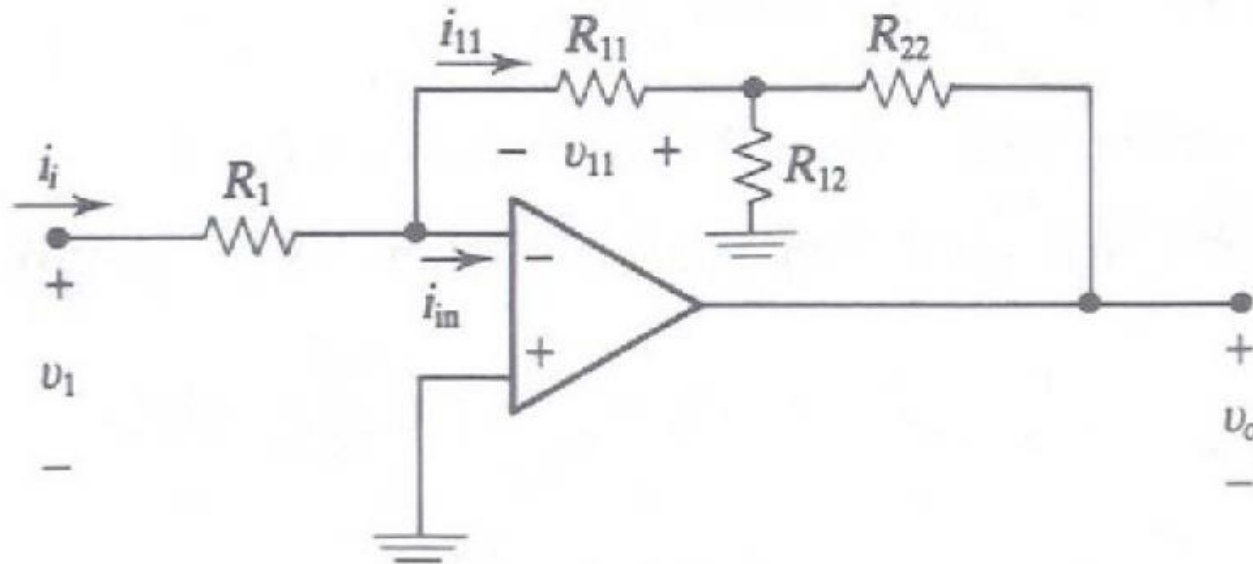



Problem (Time to solve - 10 min)

Find the gain of the circuits. Assume ideal op-amp.



Design an OpAmp circuit. Input voltage range 0.3V-1.0V output voltage 0.5 V to 4.5 V.

# Clocked RS Flip-flop

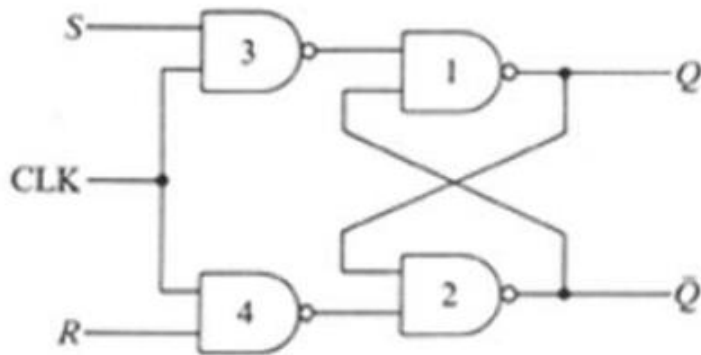


(a) Wired using NAND gates


Mode of operation	Inputs			Outputs	
	CLK	S	R	Q	$\bar{Q}$
Hold		0	0	no change	
Reset		0	1	0	1
Set		1	0	1	0
Prohibited		1	1	1	1

= positive clock pulse

(b) Truth table

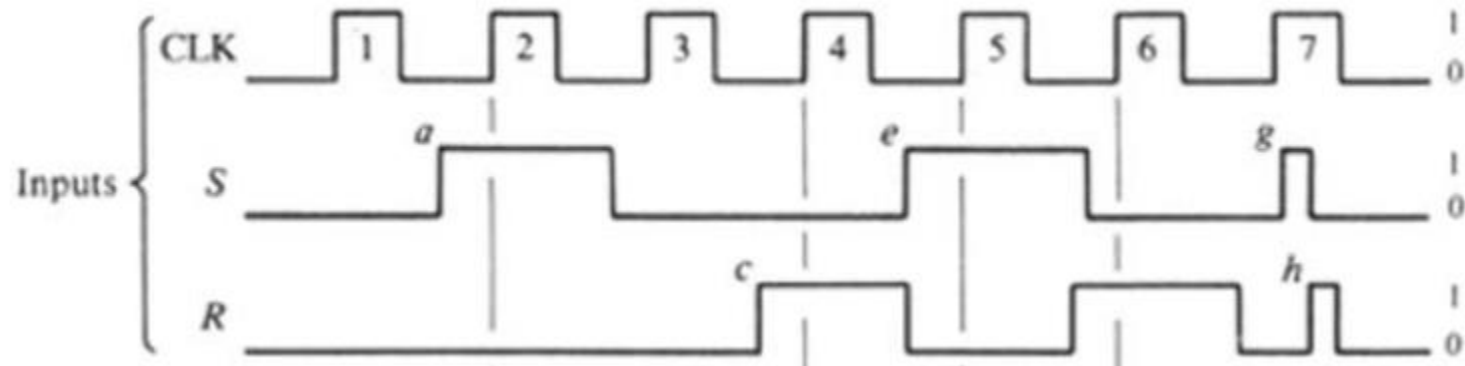

# Clocked RS Flip-flop

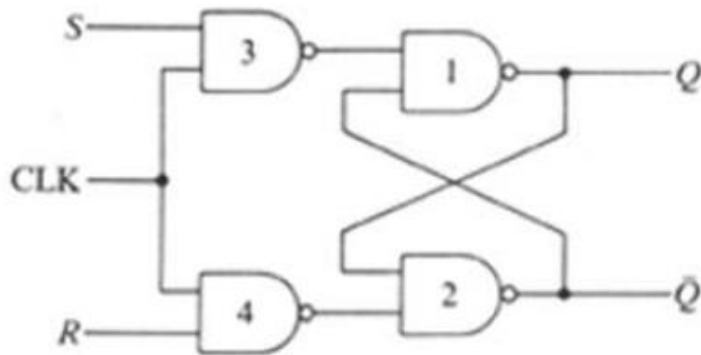


(a) Wired using NAND gates

Mode of operation	Inputs			Outputs	
	CLK	S	R	Q	$\bar{Q}$
Hold		0	0	no change	
Reset		0	1	0	1
Set		1	0	1	0
Prohibited		1	1	1	1

= positive clock pulse

(b) Truth table

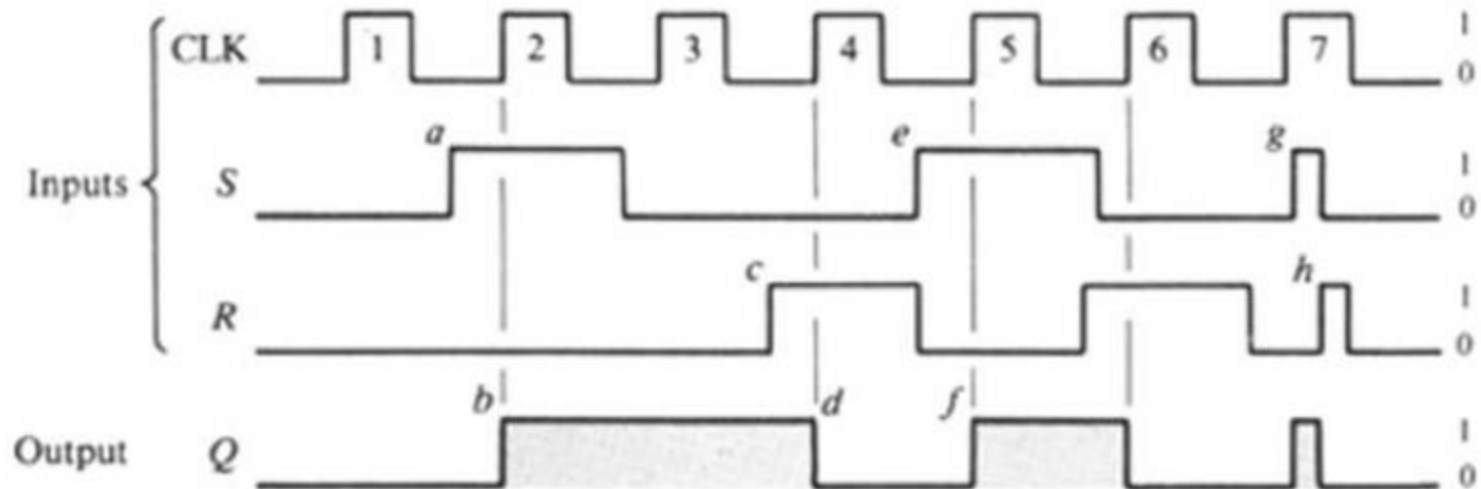

# Clocked JK Flip-flop

